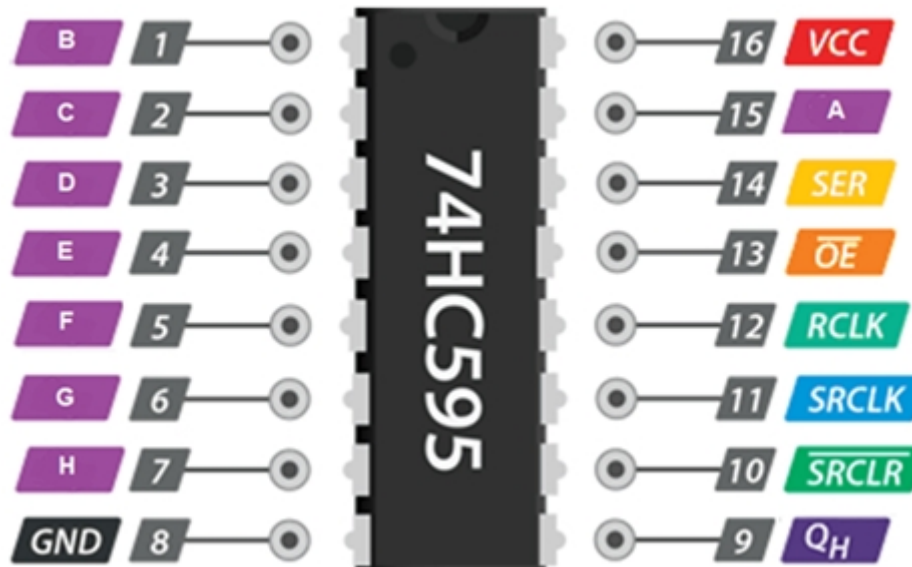


STEMKRAF - 74HC595 (Shift Register with 8-bit OUTPUT)

<https://github.com/teaksoon/stemkraf>

Each 74HC595 Shift Register IC provides 8 digital output from a single micro-controller digital output pin. Each 74HC595 chip can be "chained" to another 74HC595 chip. That means we can have multiples of 8 additional digital output pins from each "chained" 74HC595 chip. 1chip=8output, 2chips=16output, 3chips=24output and so on...



GND - To Arduino GND

VCC - To Arduino VCC

A to H - Each Pin is connected to one digital output device

SER - Connect to any Arduino Pin (only for first chip in multiple chips setup). To be set from our program to either HIGH or LOW. This will be moved into A when shifted.

SRCLK - Connect to any Arduino Pin

Used with SER, starts with LOW. When SRCLK is changed from LOW to HIGH, bit **shifting** happens, H moves to QH (G to H, F to G, ... A to B), finally the bit **SER moves into A**

RCLK - Connect to any Arduino Pin

Used with A to H. Start with LOW, When RCLK is changed from LOW to HIGH, The **A-H state(LOW or HIGH) is available to all the the output device** connected to each of them

QH - Buffer for multiple chained chips operation

The bit that got "shifted-out" by SRCLK (bit H), comes here. **To be connected to the next 74HC595 chip's SER Pin**

SRCLR - Clear entire Shift Register

When SRCLR is set to LOW, the entire Shift Register will be cleared. Normally we dont need to use this, so **we just connect to VCC(which is always HIGH)**. If required, connect to any Arduino Pin

OE - Enable or Disable A to H

When set to HIGH, A to H will be disabled. When OE is set to LOW, A-H will be enabled. Since we normally used them as enabled, **we just connect to GND(which is always LOW)**. If required, connect to any Arduino Pin

For multiple chips, they shares the **same SRCLK, RCLK** Arduino pin

STEMKRAF - 74HC595 (Shift Register for 8-bit OUTPUT)


<https://github.com/teaksoon/stemkraf>

Program: **stemkraf_74HC595**

(1/2): test program for 74HC595

:

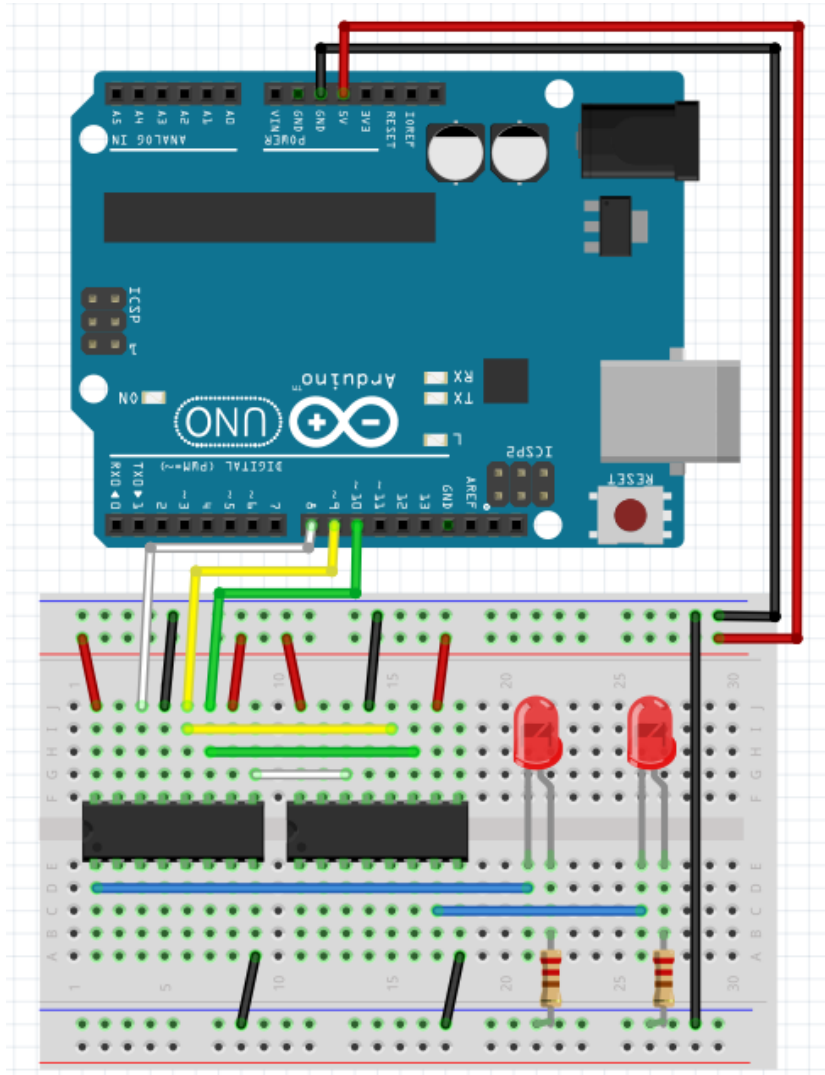: by TeakSoon Ding for STEMKRAF (NOV-2021)



Hardware:

1x Arduino Uno

1x Solderless Breadboard

Jumper wires

2x 5mm LED

2x Resistor 220ohm

2x 74HC595 Shift Register

This setup has 2 chained 74HC595 chip (you can also set up a single chip or more than 2 chained chips)

Each 74HC595 chip have 8 output pins. In this setup we have 2 chips, means we have 16 Output Pins. We only use 2 LED for Output, with 14 unused Output Pins

Each chip has output pin labelled as A to H, you can connect any digital output device to it.

The number Arduino Uno pin used is the same for 1 chip or multiple chained chips.

STEMKRAF - 74HC595 (Shift Register for 8-bit OUTPUT)

<https://github.com/teaksoon/stemkraf>


Program: **stemkraf_74HC595**

(2/2): test program for 74HC595

:

: by TeakSoon Ding for STEMKRAF (NOV-2021)

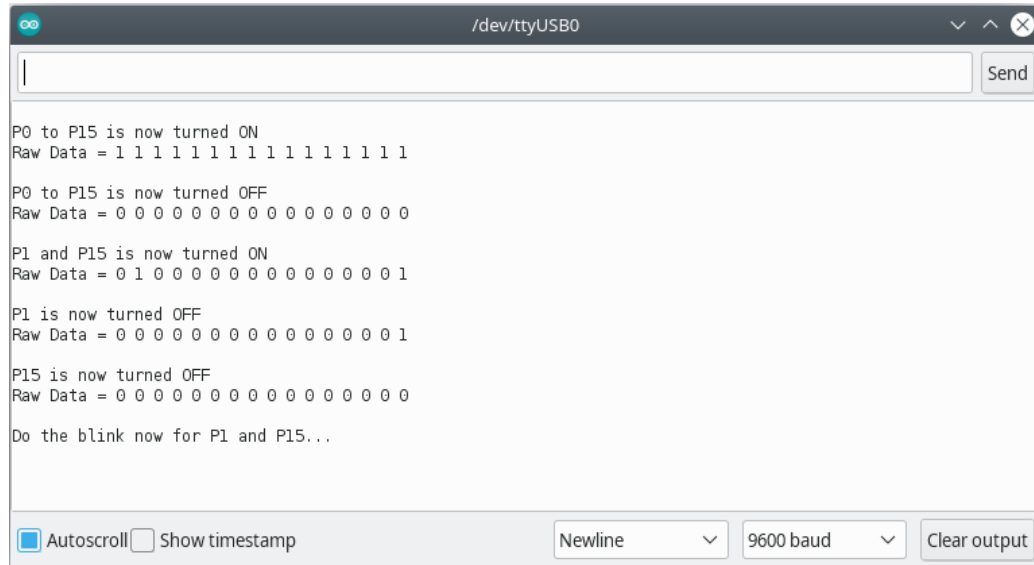- Upload this program with the Arduino IDE Software
- Open up the Serial Monitor from the Arduino IDE Software
- Watch the LED and the Serial Monitor Screen



Each output is reference by a pin index position(iPos), starting from 0 to 7 for the first chip, second chained chip 8 to 15, third chained chip 16 to 23 and so on...

8-bits for each chip. 1-bit is one index position.

There are 2 main function in this program.

sreg_set_state(iPos, pinState) - function to set the bits for individual shift register output pins, stores data in an array, wont be reflected in connected device yet until we run the **sreg_74hc595_write()** function

iPos = 0 to ... (max iPos depends on number of chips connected)
pinState = HIGH or LOW

sreg_74hc595_write() - The state of all tne chained chip pins will be reflected to the output devices, all at one go

This program uses an array of 8-bits (byte), this is to easily manage the chained chips. Each byte in the array is for each Chip. To have more chips, we only need to change **#define TOTAL_CHIP**